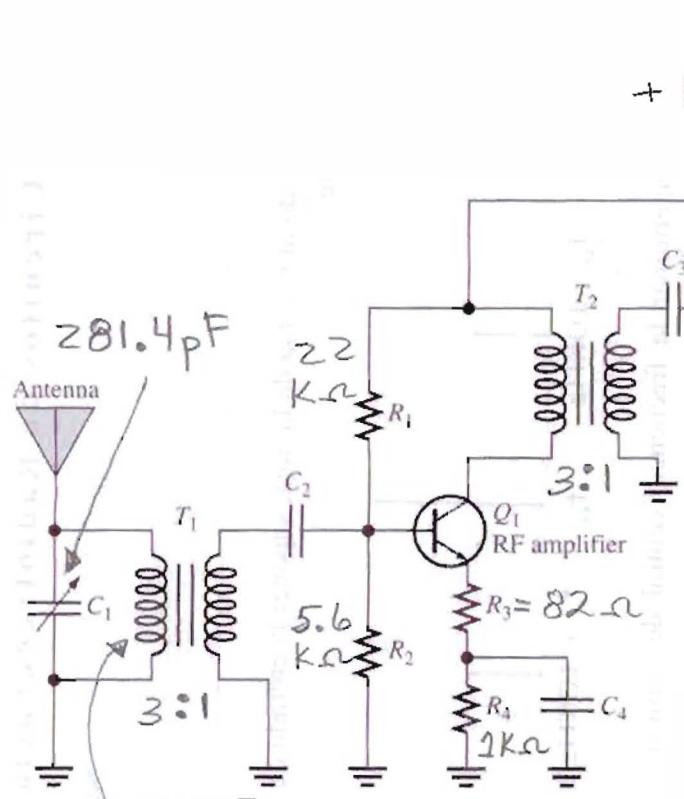


# Circuitos de Radiofrecuencia

Segundo examen parcial

Semestre 2011-2

Examen A




$$90 \mu H$$


$$R_{S0} = 3 \Omega$$

$$\beta = 150$$

$$r_o = 70 k\Omega$$

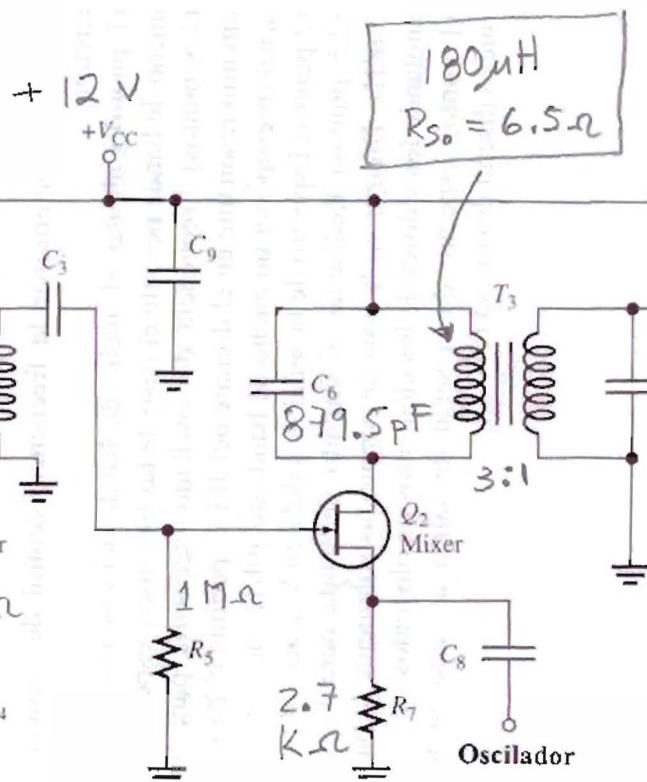

$$g_m = 3000 \mu S$$

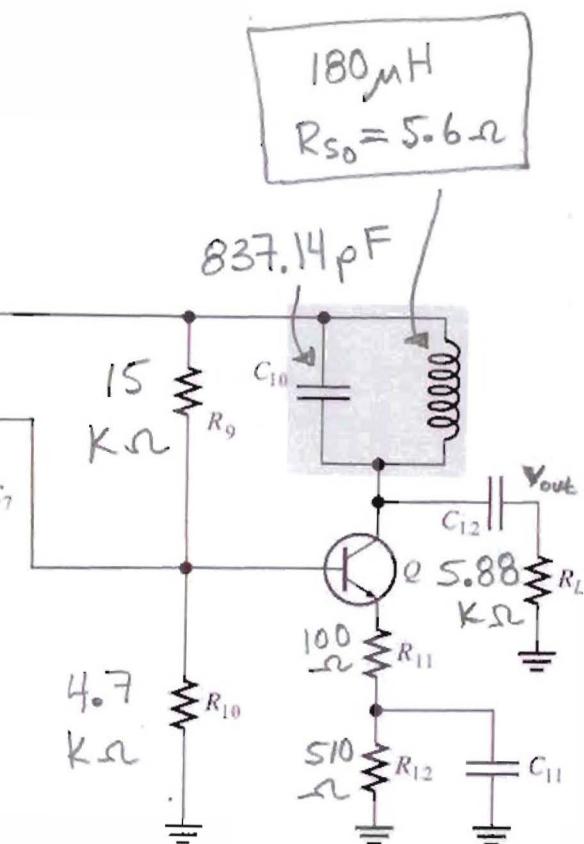

$$\beta = 150$$

$$r_o = 70 k\Omega$$

$$180 \mu H$$

$$R_{S0} = 5.6 \Omega$$