
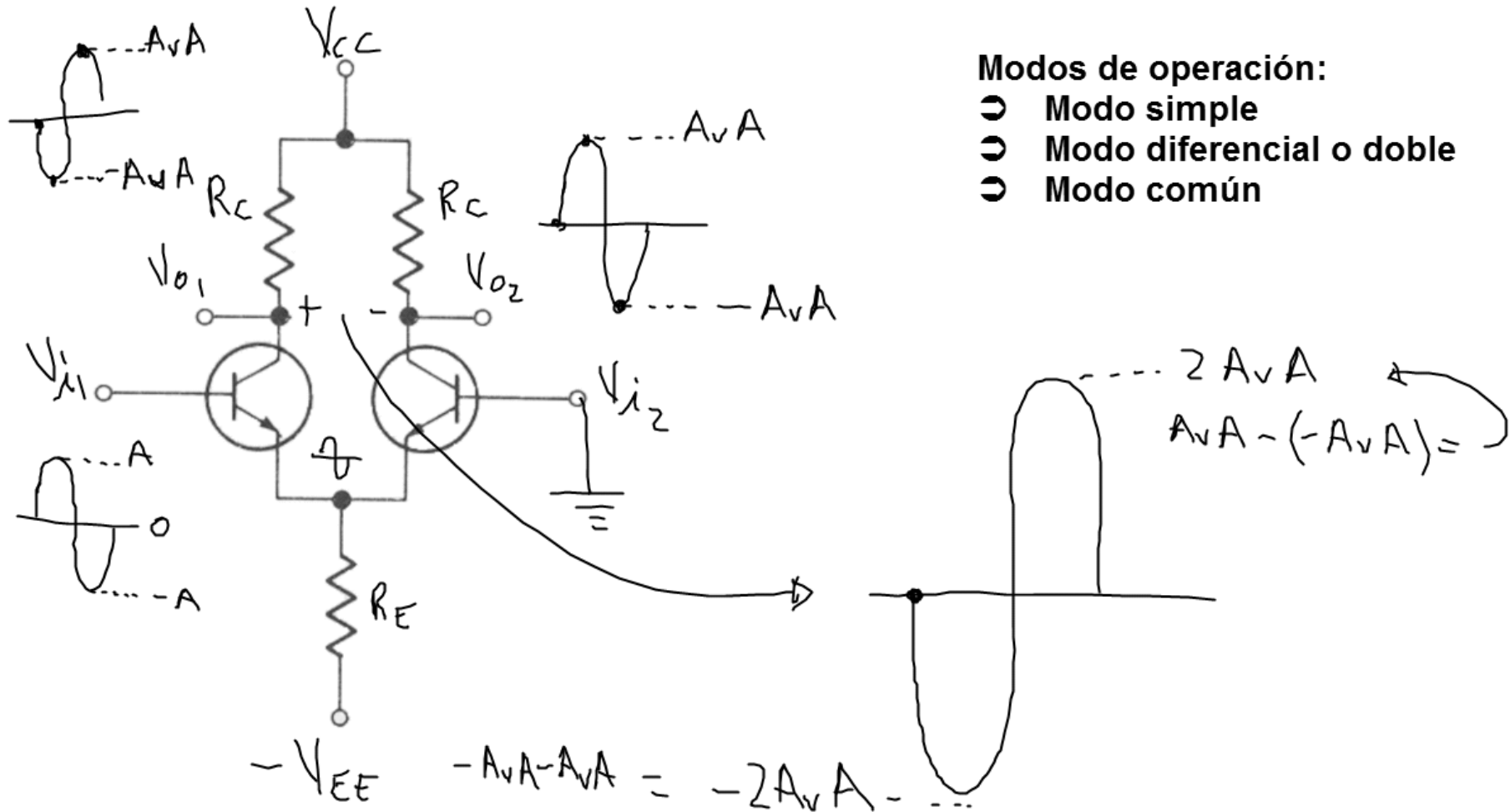


Amplificadores diferenciales

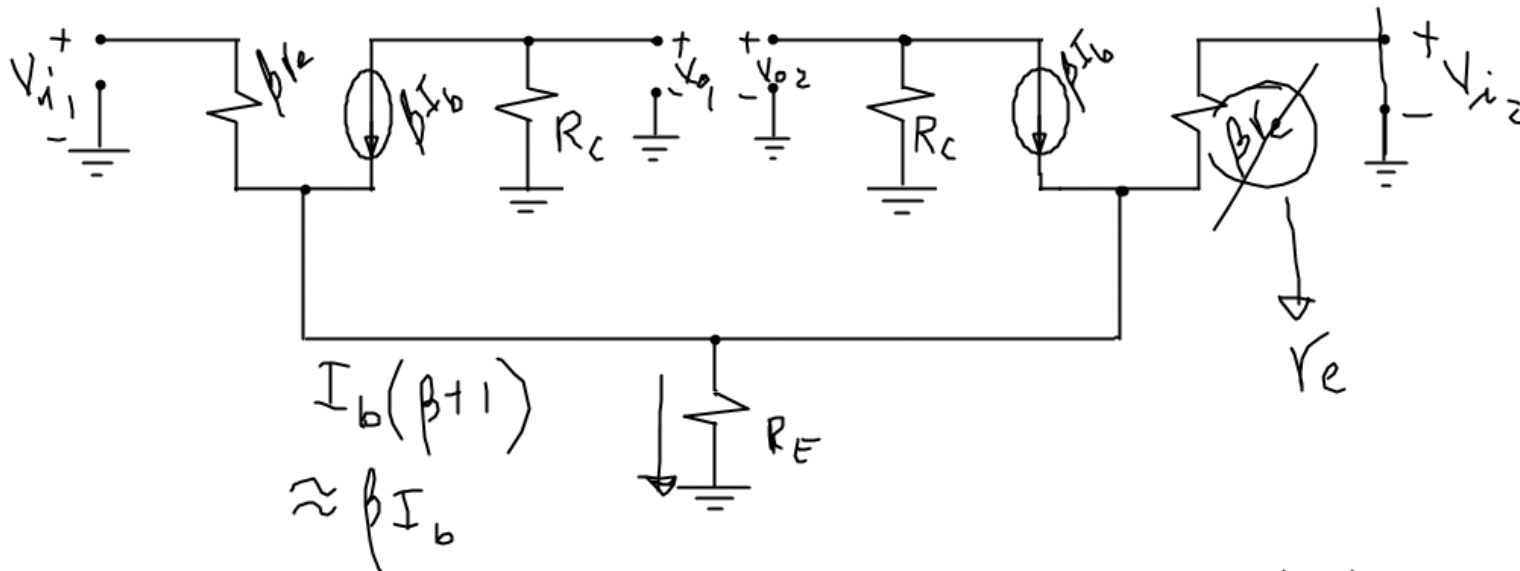


Análisis en AC
Modo simple y modo diferencial



Modo simple

$$A_v = \frac{V_o}{V_i} = \frac{\beta I_b R_c}{I_b \beta r_e + \beta I_b r_e} = \frac{R_c}{2 r_e}$$

Análisis en AC
Modo común

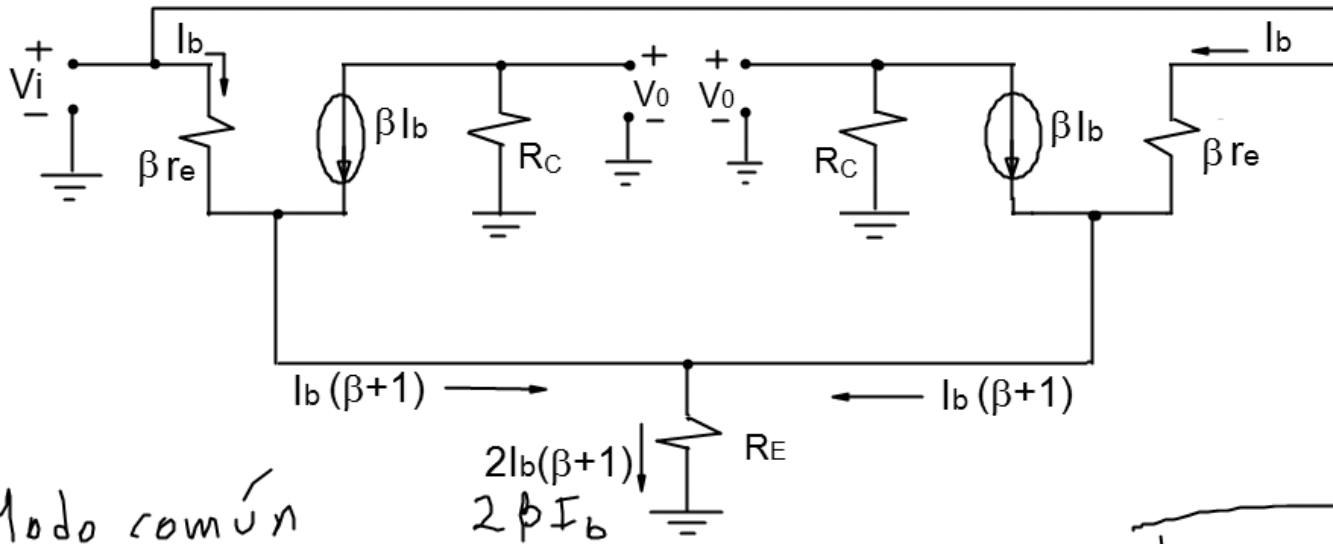


Modo común


$$A_c = \frac{V_o}{V_{ic}} = \frac{\beta I_b R_c}{I_b \beta r_e + 2\beta I_b R_E} = \frac{R_c}{r_e + 2R_E}$$

$$V_{ic} = \frac{1}{2} (V_{i1} + V_{i2})$$

$$r_o (r_o + R_E)$$

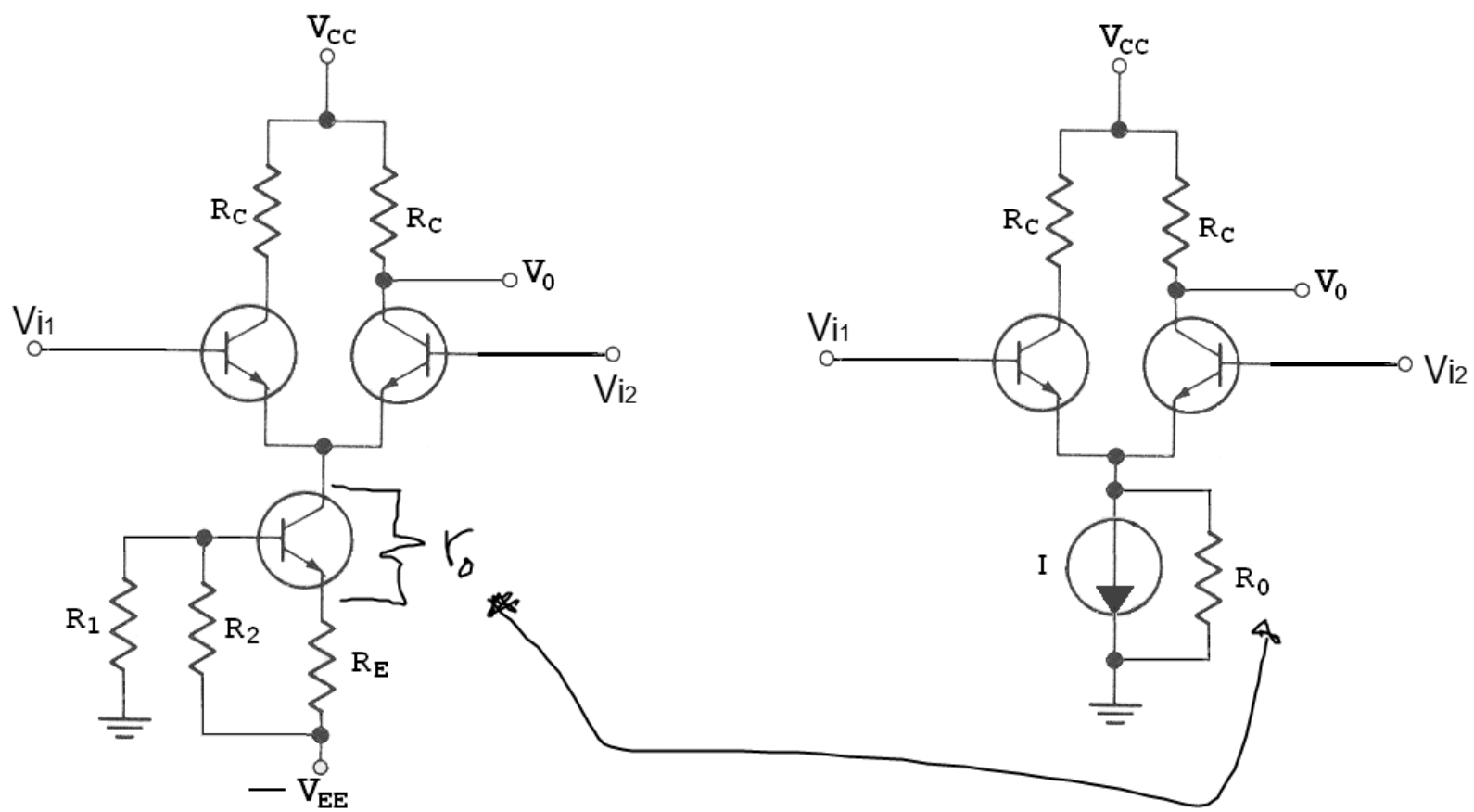

Ejemplo:

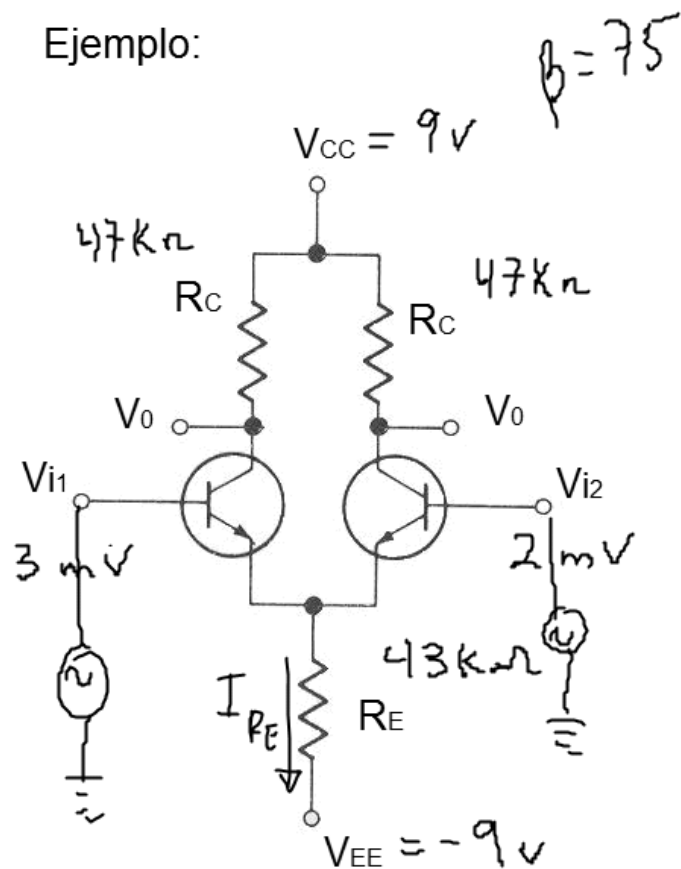

$$I_{RE} = \frac{V_{EE} - 0.7V}{R_E} = \frac{9 - 0.7}{43k\Omega}$$

$$I_{RE} = 193\mu A$$

$$I_E = \frac{1}{2} I_{RE} = 96.5\mu A$$

$$r_e = \frac{26mV}{I_E} = 269\Omega$$


$$A_v = \frac{R_C}{2r_e} = \frac{47k\Omega}{2(269)} = 87.4 = A_d$$

$$A_c = \frac{R_C}{r_e + 2R_E} = \frac{47k\Omega}{269 + 2(43k\Omega)} = 0.54$$

Modo diferencial

$$V_{o1} = A_v V_d = (87.4)(V_{i1} - V_{i2}) = (87.4)(3mV - 2mV) = 87.4mV$$

Ejemplo

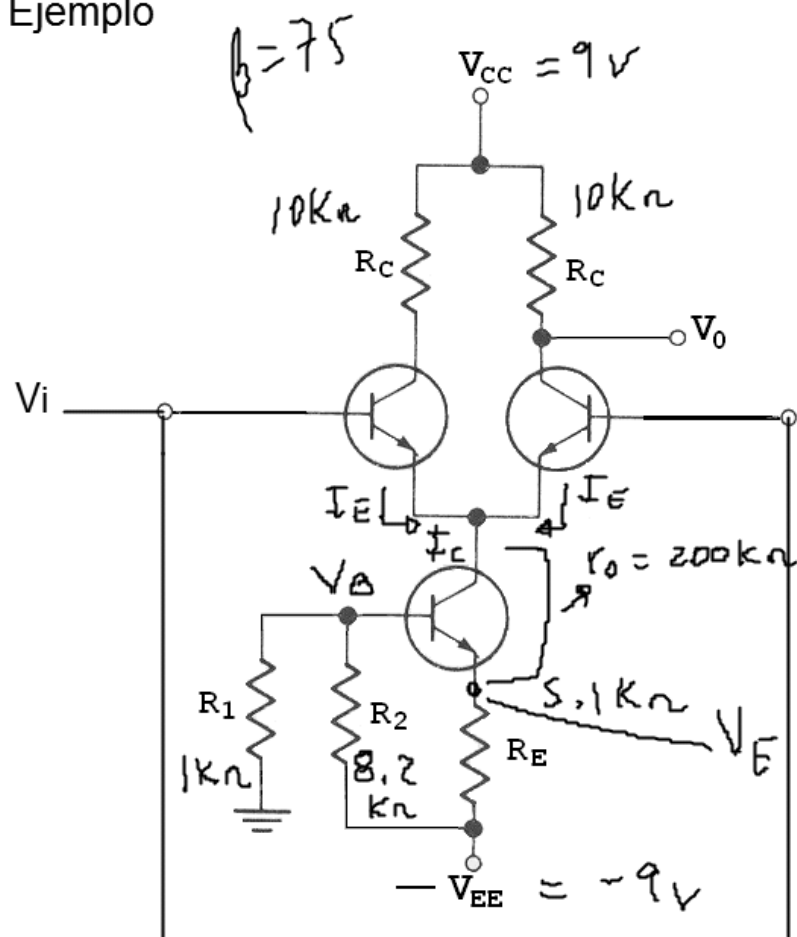

$$V_{R_1} = \frac{1k\Omega}{1k\Omega + 8.2k\Omega} (-9)$$

$$V_{R_1} = -0.978V = V_B$$

$$V_{BE} = V_B - V_E$$

$$V_E = V_B - V_{BE}$$

$$V_E = -0.978 - 0.7$$

$$V_E = -1.678V$$


$$V_{RE} = V_E - V_{EE} = -1.678 - (-9)$$

$$V_{RE} = 7.322V = I_{RE} R_E$$

$$I_{RE} = \frac{7.322}{5.1k\Omega} \approx 1.44mA$$

Ejemplo:

$$r_o = 100 \text{ k}\Omega$$

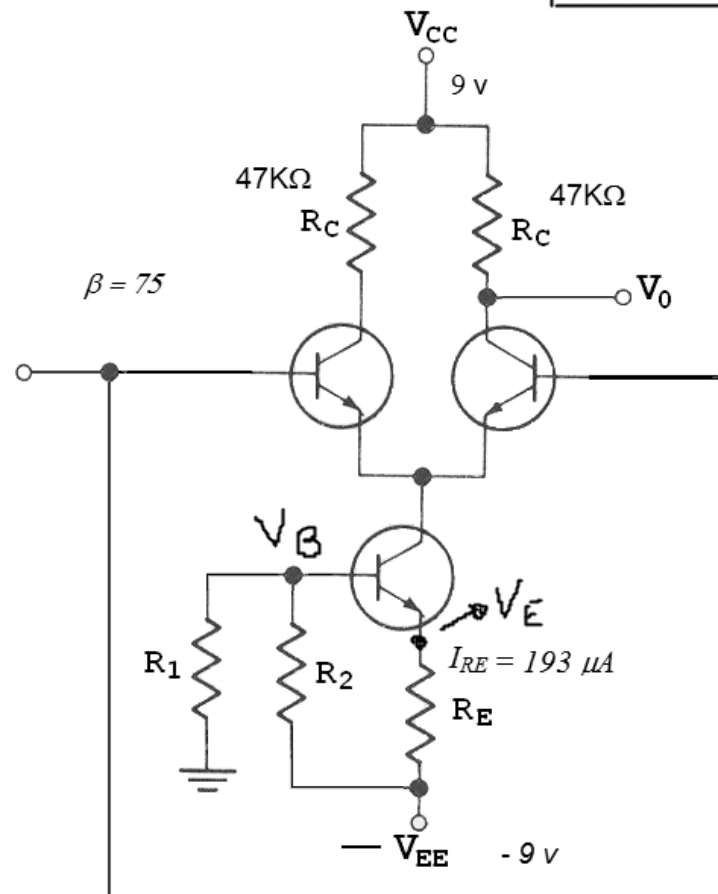

$$\beta R_E \geq 10 R_1$$

$$R_1 = R_2$$

$$V_{R_1} = \frac{R_1}{R_1 + R_2} (-9)$$

$$V_{R_1} = -4.5 \text{ V} = V_B$$

$$V_E = V_B - V_{BE}$$

$$V_E = -4.5 \text{ V} - 0.7 \text{ V} = -5.2 \text{ V}$$

$$V_{RE} = V_E - V_{EE} = -5.2 - (-9) = 3.8 \text{ V}$$

$$R_E = \frac{V_{RE}}{I_{RE}} = \frac{3.8 \text{ V}}{193 \mu\text{A}} = 19689 \approx 20 \text{ k}\Omega$$

